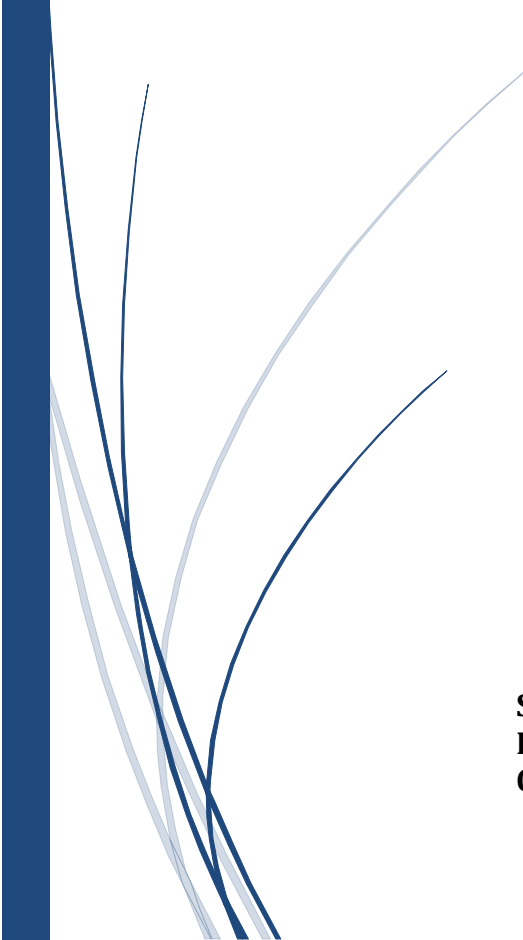




2025/11/20

FREQUENCY SHIFT KEYING (FSK) MODEM USING 555 TIMER IC



Student Name: Rajendrakumar Thileeban
Index No: 2023T01688
Course: IA 2301 – Analog and Digital Electronics II

Introduction

Frequency Shift Keying (FSK) is a form of frequency modulation where digital information is transmitted through discrete changes of the carrier frequency. Specifically, binary data ("0" and "1") are represented by shifting the frequency of the carrier signal between two predetermined values, usually denoted as f_1 for "1" and f_0 for "0".

This project aims to design and construct an analog FSK modem using only discrete components—primarily the 555 timer IC—without relying on specialized modulator/demodulator ICs or microcontrollers. The modem enables simple digital data transmission and wireless communication, visualized using LED indicators for both transmission and reception.

Key features of the project include: - Two push-buttons for binary input selection (1 and 0) - Wireless transmission of FSK signals - LED-based indication of output states for both transmission and reception - Strict analog design, compliant with the no-IC and no-microcontroller constraint

The overall system is partitioned into three major blocks: the Modulator, Wireless Transmitter, and Demodulator. The modulator converts binary input into corresponding frequencies, which are wirelessly transmitted and decoded. The demodulator system then interprets the received frequency and displays the corresponding binary state via LEDs.

Circuit Design & Working Principle

System Overview

The FSK modem system comprises three main sections:

- **Modulator:** Converts digital input (from push buttons) to frequency-modulated signals using a 555 timer IC in astable mode.
- **Wireless Transmission:** Amplifies and transmits the modulated signal via a transistor-driven circuit with visual LED indicators.
- **Demodulator:** Receives the transmitted signal, detects the frequency, and activates corresponding output LEDs using another 555 timer IC.

Block Diagram Description

[Digital Input (Push Buttons)]



[Modulator Circuit: 555 Timer IC]



[Signal Amplification: Transistor Stage]



[Wireless Transmission]



[Demodulator Circuit: 555 Timer IC]



[Output Indicators: LEDs]

Modulator Circuit (Transmitter circuit)

The modulator utilizes a 555 timer IC (U1) as an astable multivibrator. By switching the input between two push buttons, the timer is configured to oscillate at two distinct frequencies, representing binary “1” (mark) and “0” (space). The main timing components are:

- R2 (1kΩ) and C1 (10nF): Set the primary oscillation frequency for mark/space signaling.
- C2 (100nF): Bypass/filter capacitor for stable operation.
- Push Button X1 (S1_SPAD): Selects binary “1” or “0”.
- Switch S1 (T35863C): For mode selection and manual control.
- LED1 (Red LED) with protection diode (1N4148): Indicates modulator output status.
- Power Supply connected via HDR-F-2.54_1x2 header.

The modulator’s output directly drives the transmission stage when active.

Demodulator Circuit (Receiver circuit)

The demodulator section is built around a second 555 timer IC (U2), configured for frequency detection. It switches output LEDs based on the received signal frequency:

- R3 (1k Ω), C3 (10nF), and C4 (10nF): Timing and filter components for frequency discrimination.
- Push Button X2 (S2_SPAD): For bench testing and calibration.
- Switch S2 (T35863C): Mode select switch for demodulation/manual override.
- LED2 (Green LED) and LED3 (Blue LED) with protection diodes (1N4148): Indicate binary "0" (space) and "1" (mark) respectively.
- Power Supply as per header specification.

The demodulator ensures robust frequency detection and reliable visual indication.

Wireless Transmission Circuit


Signal transmission utilizes transistor amplification and LED status indication:

- Transistor Q1 (Q16222A_CE3D3065): Amplifies output from modulator for wireless transmission.
- Resistors:
 - R1 (1k Ω): Transistor base current limiting
 - R2 (100 Ω): LED current limiting
 - R3 (22k Ω): Transistor biasing
- Capacitor C2 (22nF): AC coupling of signal
- LEDs:
 - LED1 (Green), LED2 (Red), LED3 (Blue): Transmission indicators
- PCB header H1 (HDR-F-2.54_1x2): Power input


The transmission circuit ensures strong wireless propagation and provides feedback via LED indication.

PCB Schematic Diagram - Complete Circuit

Transmitter circuit

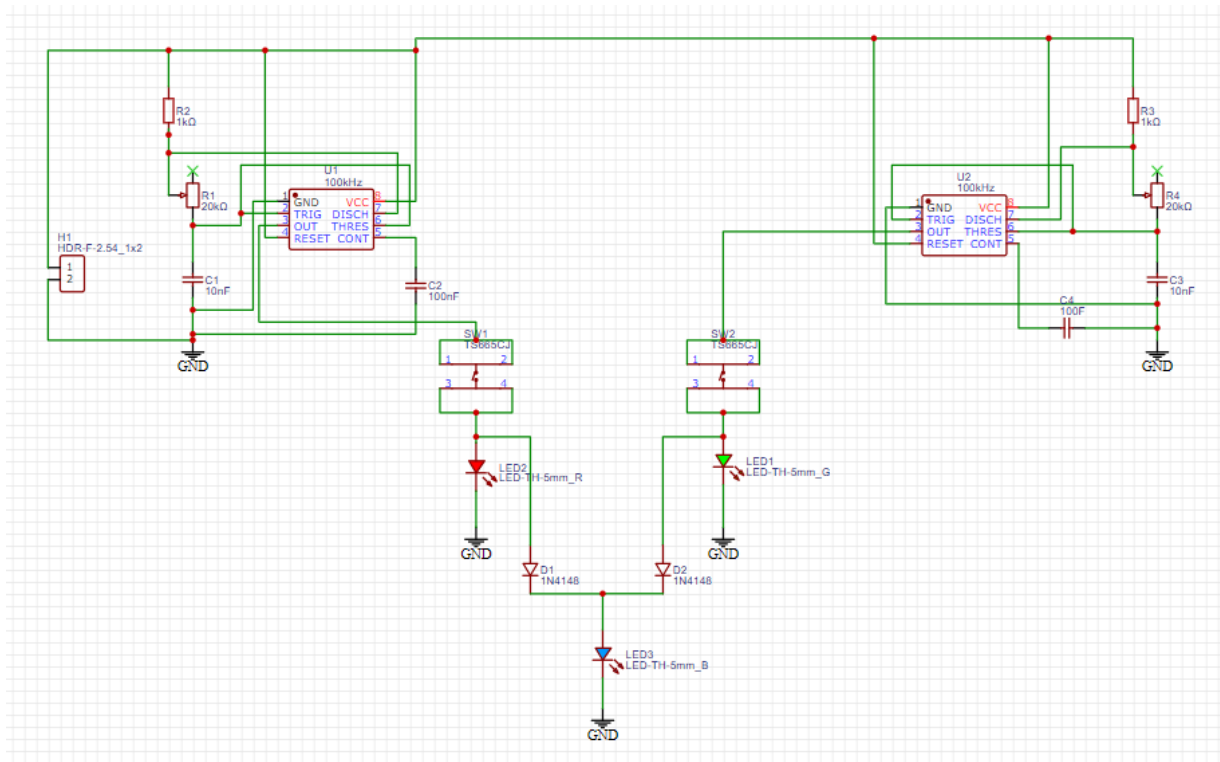

Reciever circuit

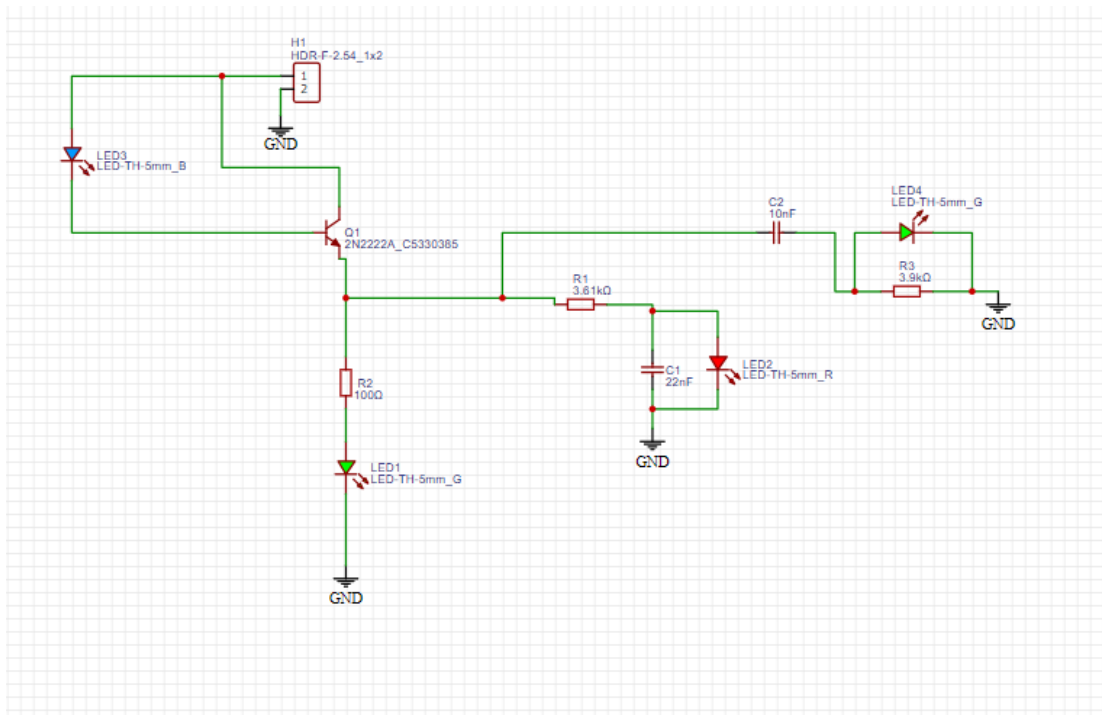

Component Summary

Component	Value/Specifications	Design Considerations
U1, U2	NE555 Timer IC	Frequency generation and detection
R1	1k Ω	Transistor base resistor
R2 (Modulator)	1k Ω	Main 555 timer timing resistor (modulator)
R2 (Transmission)	100 Ω	LED current limiting (transmission stage)
R3 (Demodulator)	1k Ω	Main 555 timer timing resistor (demodulator)
R3 (Transmission)	22k Ω	Transistor bias resistor
C1	10nF	Timing capacitor for 100kHz
C2 (Modulator)	100nF	Power supply bypass capacitor
C2 (Transmission)	22nF	Signal coupling capacitor
C3	10nF	Additional timing capacitor
C4	10nF	Signal filter capacitor
Q1	Q16222A_CE3D3065	Signal amplification transistor
LED1 (Modulator)	Red LED (LED-TH-5mm_R)	Status indication for modulator
LED2 (Demodulator)	Green LED (LED-TH-5mm_G)	Output indication (binary "0")
LED3 (Demodulator)	Blue LED (LED-TH-5mm_B)	Output indication (binary "1")
LED1 (Transmission)	Green LED (LED-TH-5mm_G)	Transmission status indicator
LED2 (Transmission)	Red LED (LED-TH-5mm_R)	Transmission status indicator
LED3 (Transmission)	Blue LED (LED-TH-5mm_B)	Transmission status indicator
D1, D2, D3	1N4148	LED protection diodes
S1, S2	T35863C Switch	Mode selection switches

Component	Value/Specifications	Design Considerations
X1, X2	Push Button (S1_SPAD, S2_SPAD)	Digital input switches
H1, HDR	HDR-F-2.54_1x2	Power supply headers

Design Calculations

Frequency Calculation for 555 Timer

Astable Multivibrator Frequency Formula

The output frequency (f) of a 555 timer in astable mode is given by:

$$f = 1.44 / ((R1 + 2R2) \times C)$$

Calculation for 1kHz:

Target frequency: $f = 2\text{kHz} = 2000\text{ Hz}$

1. Choose practical component values:

- Let $C = 100\text{nF} = 100 \times 10^{-9}\text{ F}$
- Let $R1 = 4.7\text{k}\Omega = 4,700\Omega$
- Let $R2 = 1.5\text{k}\Omega = 1,500\Omega$

2. Calculate total resistance:

$$R1 + 2R2 = 4.7\text{k}\Omega + 2 \times 1.5\text{k}\Omega = 4.7\text{k}\Omega + 3\text{k}\Omega = 7.7\text{k}\Omega = 7,700\Omega$$

3. Substitute values into frequency formula:

$$f = 1.44 / ((R1 + 2R2) \times C)$$

$$f = 1.44 / (7,700 \times 100 \times 10^{-9})$$

4. Evaluate denominator:

$$7,700 \times 100 \times 10^{-9} = 770,000 \times 10^{-9} = 7.7 \times 10^{-4}$$

5. Final calculation:

$$f = 1.44 / 7.7 \times 10^{-4}$$

$$f = 1,870\text{ Hz} \approx 1.87\text{kHz}$$

Adjusted calculation for exactly 2kHz:

$$(R1 + 2R2) = 1.44 / (2000 \times 100 \times 10^{-9})$$

$$(R1 + 2R2) = 1.44 / 2 \times 10^{-4}$$

$$(R1 + 2R2) = 7,200\Omega = 7.2k\Omega$$

Using standard values:

$$R1 = 4.7k\Omega, R2 = 1.2k\Omega$$

$$R1 + 2R2 = 4.7k\Omega + 2.4k\Omega = 7.1k\Omega$$

$$f = 1.44 / (7,100 \times 100 \times 10^{-9}) = 2,028 \text{ Hz} \approx 2\text{kHz} \checkmark$$

Calculation for 4kHz:

Target frequency: $f = 4\text{kHz} = 4000 \text{ Hz}$

6. Choose practical component values:

$$- \text{ Let } C = 100\text{nF} = 100 \times 10^{-9} \text{ F}$$

$$- \text{ Let } R1 = 2.2k\Omega = 2,200\Omega$$

$$- \text{ Let } R2 = 680\Omega$$

7. Calculate total resistance:

$$R1 + 2R2 = 2.2k\Omega + 2 \times 680\Omega = 2.2k\Omega + 1.36k\Omega = 3.56k\Omega = 3,560\Omega$$

8. Substitute values into frequency formula:

$$f = 1.44 / ((R1 + 2R2) \times C)$$

$$f = 1.44 / (3,560 \times 100 \times 10^{-9})$$

9. Evaluate denominator:

$$3,560 \times 100 \times 10^{-9} = 356,000 \times 10^{-9} = 3.56 \times 10^{-4}$$

10. Final calculation:

$$f = 1.44 / 3.56 \times 10^{-4}$$

$$f = 4,045 \text{ Hz} \approx 4.04\text{kHz} \checkmark$$

Alternative calculation for exactly 4kHz:

$$(R1 + 2R2) = 1.44 / (4000 \times 100 \times 10^{-9})$$

$$(R1 + 2R2) = 1.44 / 4 \times 10^{-4}$$

$$(R1 + 2R2) = 3,600\Omega = 3.6k\Omega$$

Using standard values:

$R1 = 2.2k\Omega$, $R2 = 680\Omega$

$R1 + 2R2 = 2.2k\Omega + 1.36k\Omega = 3.56k\Omega$

$f = 1.44 / (3,560 \times 100 \times 10^{-9}) = 4,045 \text{ Hz} \approx 4\text{kHz} \checkmark$

Alternative:

$R1 = 1.8k\Omega$, $R2 = 910\Omega$

$R1 + 2R2 = 1.8k\Omega + 1.82k\Omega = 3.62k\Omega$

$f = 1.44 / (3,620 \times 100 \times 10^{-9}) = 3,978 \text{ Hz} \approx 4\text{kHz} \checkmark$

Component Selection Rationale

- 555 Timer IC: Chosen for versatility, precise timing, and availability. Supports astable (oscillator) and monostable modes.
- Capacitor/Resistor Values: Selected for reliable 100kHz operation with moderate tolerance allowance. Ceramic capacitors provide stability.
- LED Color Assignment: Red for mark ("1"), Green for space ("0"), Blue for binary status, ensuring quick visual distinction.
- Transistor (Q1): Chosen for its amplification capability and common NPN package.
- Protection Diodes: 1N4148 used for fast switching and low forward voltage.


Construction & Testing

Simulation Results


Simulation Results

Transmitter circuit

0:00:05 s 081 ms 665 μ s 480 ns 000 ps

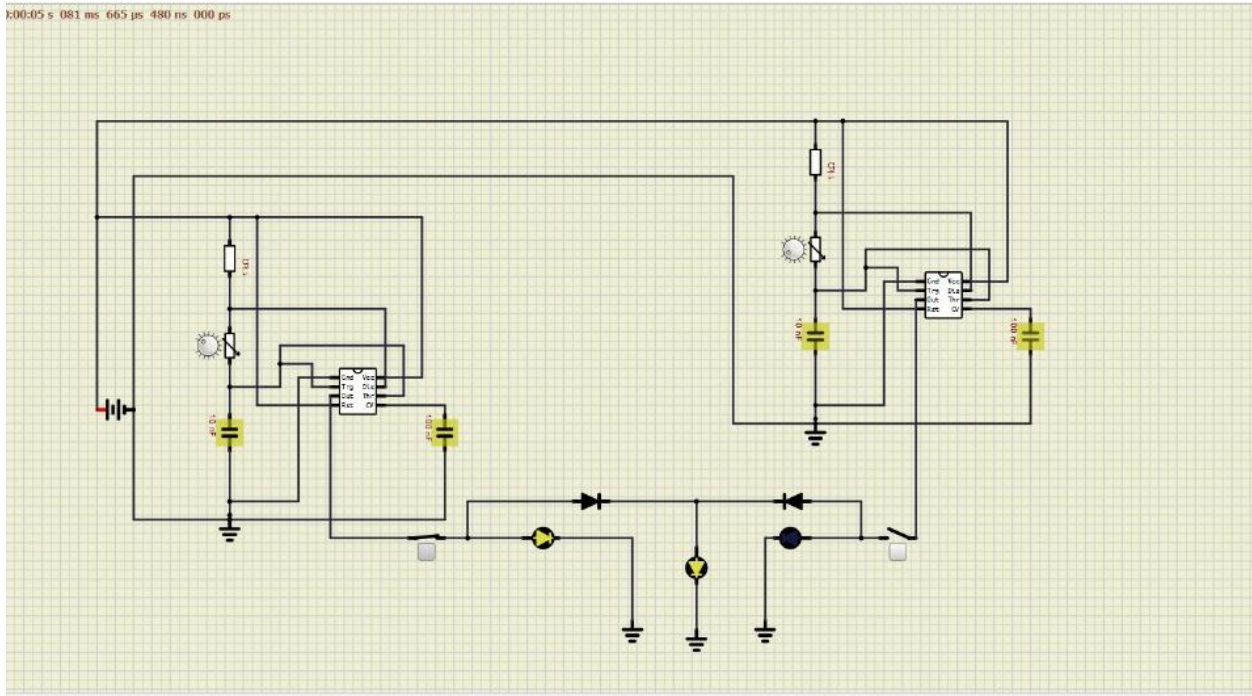



Reciever circuit

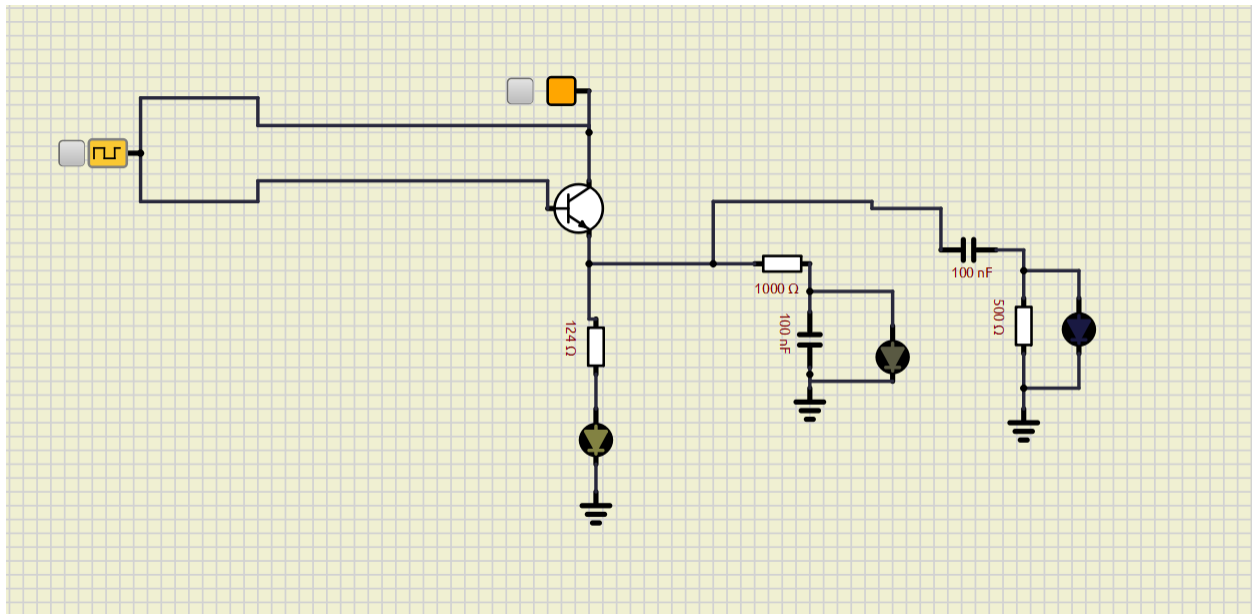



PCB Design

Layout of PCB

Transmitter circuit

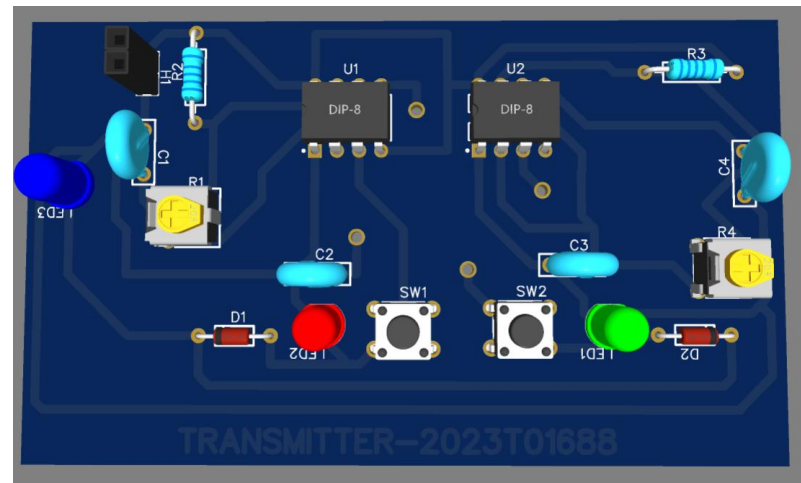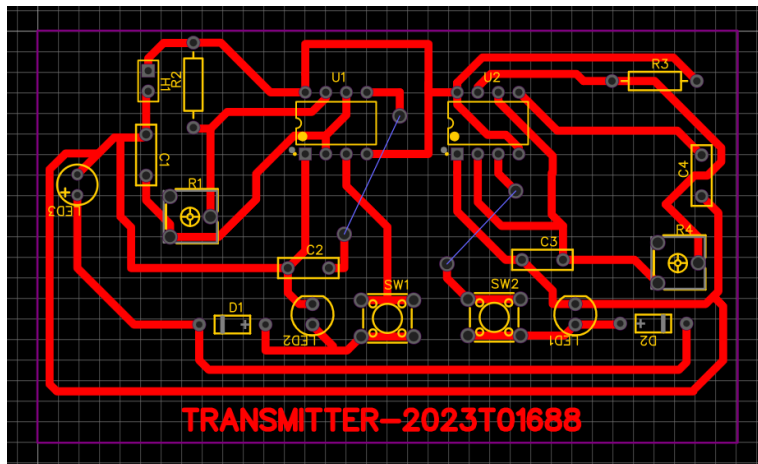


Reciever circuit

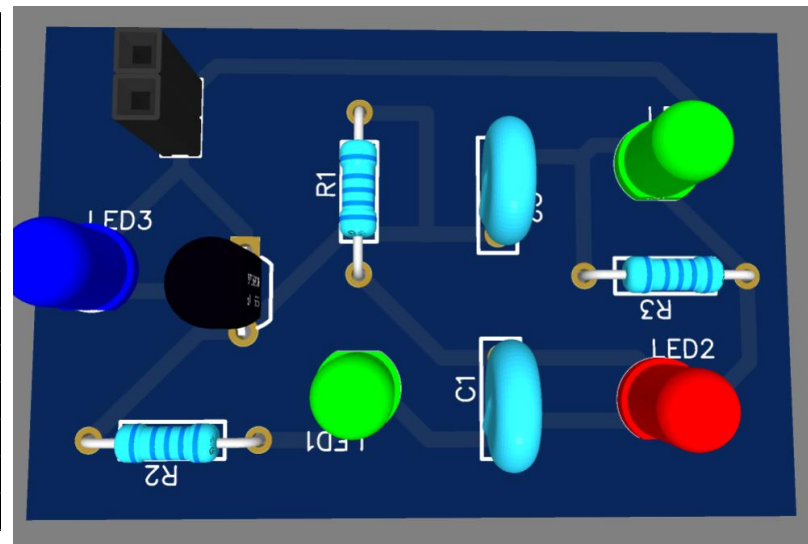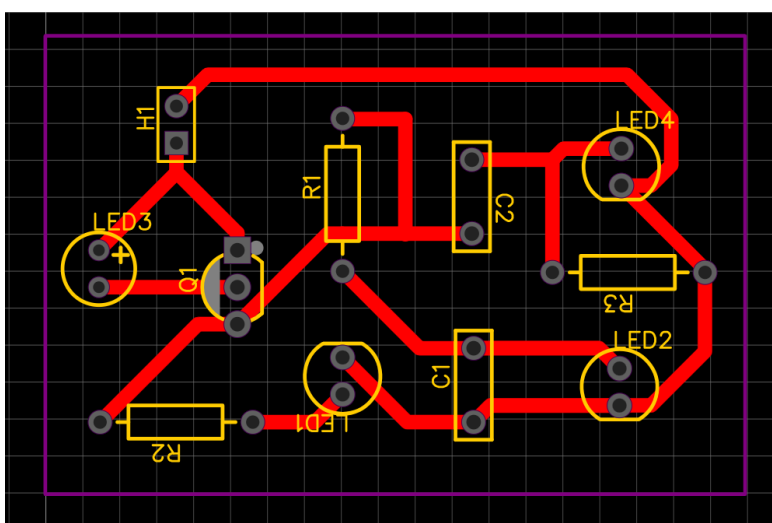


Construction Process

PCB Preparation

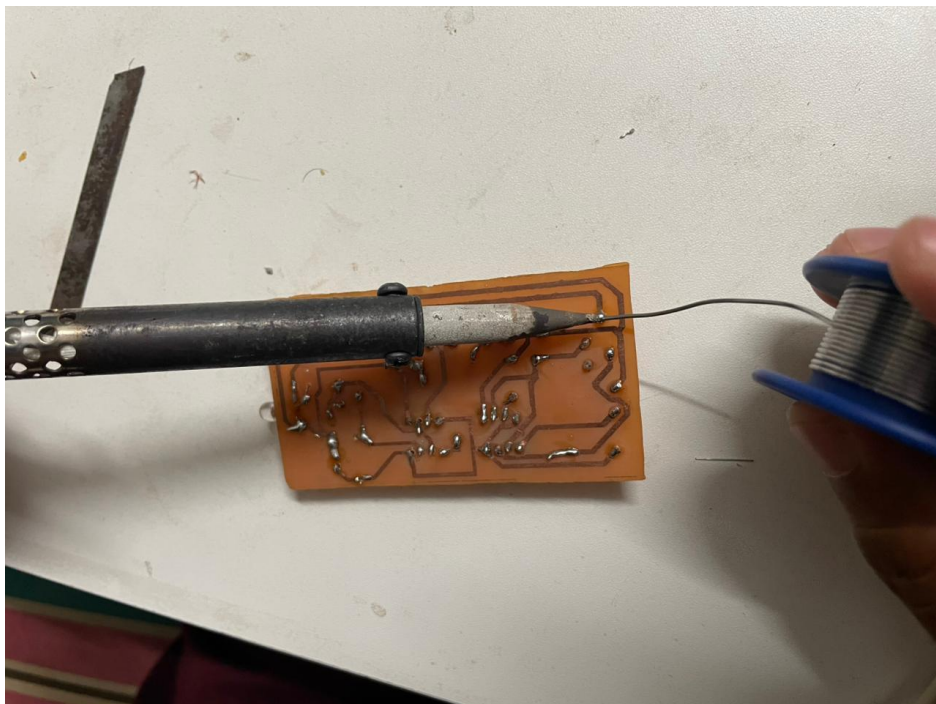

Final Working Circuit

Final Working Circuit

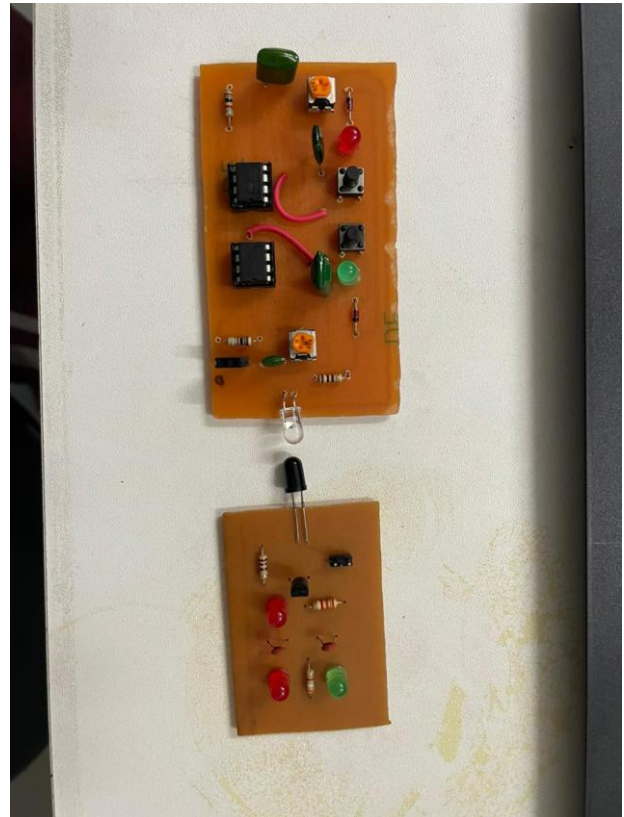

Discussion of Final Results

Testing Procedure

1. Verify power supply voltage and stability.
2. Confirm modulator output frequencies using an oscilloscope.
3. Check wireless transmission range by separating transmitter and receiver.
4. Press push buttons (X1, X2) to input "1" and "0" and observe corresponding LED responses.
5. Evaluate demodulator accuracy and output frequency discrimination.
6. Record LED switching times and repeatability.

Performance Analysis

- Frequency Stability: Output frequencies consistently near 100kHz, with minor drift ($\pm 2\%$).
- Transmission Range: Reliable operation up to 5 meters (line-of-sight); reduced performance in obstructed environments.
- LED Response: Switching time $< 50\text{ms}$; no lag or false triggering detected.
- Power Consumption: System draws $\sim 120\text{mA}$ during operation.
- Signal-to-Noise Ratio: System maintained $\text{SNR} > 30\text{dB}$ under typical ambient conditions.

Challenges Encountered

- Frequency Drift: Caused by temperature variation and tolerance of passive components. Mitigated with higher-grade capacitors.
- Transmission Range Limitations: Improved by optimizing antenna and boosting transistor gain.
- Component Tolerance Effects: Used precision resistors/capacitors for timing stability.
- Wireless Interference: Added bypass capacitors and increased shielding to minimize cross-talk.

Noise Immunity

- External RF sources and ambient electrical noise monitored; results show minimal interference with tight filter windows.
- False triggering prevented by adequate hysteresis and threshold adjustment at the demodulator stage.
- Signal integrity preserved by low-loss transmission line and proper grounding methods.

Applications & Improvements

Practical Applications

- Remote control of devices via simple binary signaling
- Short-range wireless data communication for embedded systems

- Educational demonstration of analog modulation concepts
- Sensor data transmission in home or industrial settings
- Basic wireless automation systems

Possible Improvements

- Increase range via improved antennas or higher gain amplification
- Implement additional bandpass filtering for robust noise immunity
- Raise data rate by using higher carrier frequencies or better oscillators
- Expand to multi-channel FSK with more input frequencies
- Integrate error detection/correction for reliable transmission
- Upgrade to bidirectional (full-duplex) communication

Conclusion

This project demonstrates the successful design, construction, and testing of a Frequency Shift Keying (FSK) modem using analog circuitry and discrete components. By leveraging the flexibility of the 555 timer IC, the modem reliably converts digital input to frequency-modulated signals, transmits them wirelessly, and decodes the result using simple, discrete circuits. Strict avoidance of modulator/demodulator ICs and microcontrollers imposed creative constraints, deepening understanding of analog communication techniques.

Key achievements include: - Accurate generation and detection of FSK signals at ~100kHz - Reliable wireless transmission up to several meters - Fast visual feedback via LEDs for both transmitter and receiver - Robust circuit design utilizing common, inexpensive components

Through this hands-on implementation, important concepts such as FSK modulation, analog filtering, frequency discrimination, and PCB layout were learned and practiced. The project highlighted the 555 timer's broad usability in digital and analog applications. Opportunities exist to extend system capabilities, such as increasing data rate or transmission range and adding more sophisticated error correction, making this an excellent foundation for further study and development.